

[Next](#)[Up](#)[Previous](#)[Contents](#)

Next: [Amplifier Model](#) Up: [Passive RCL Filters](#) Previous: [Passive RCL Filters](#)

Series RCL Circuit

Consider the *RCL* circuits as shown in figure 3.9. Each has a low-frequency and high-frequency approximation. Considering the band-reject filter (figure 3.6d) we obtain for the transfer function

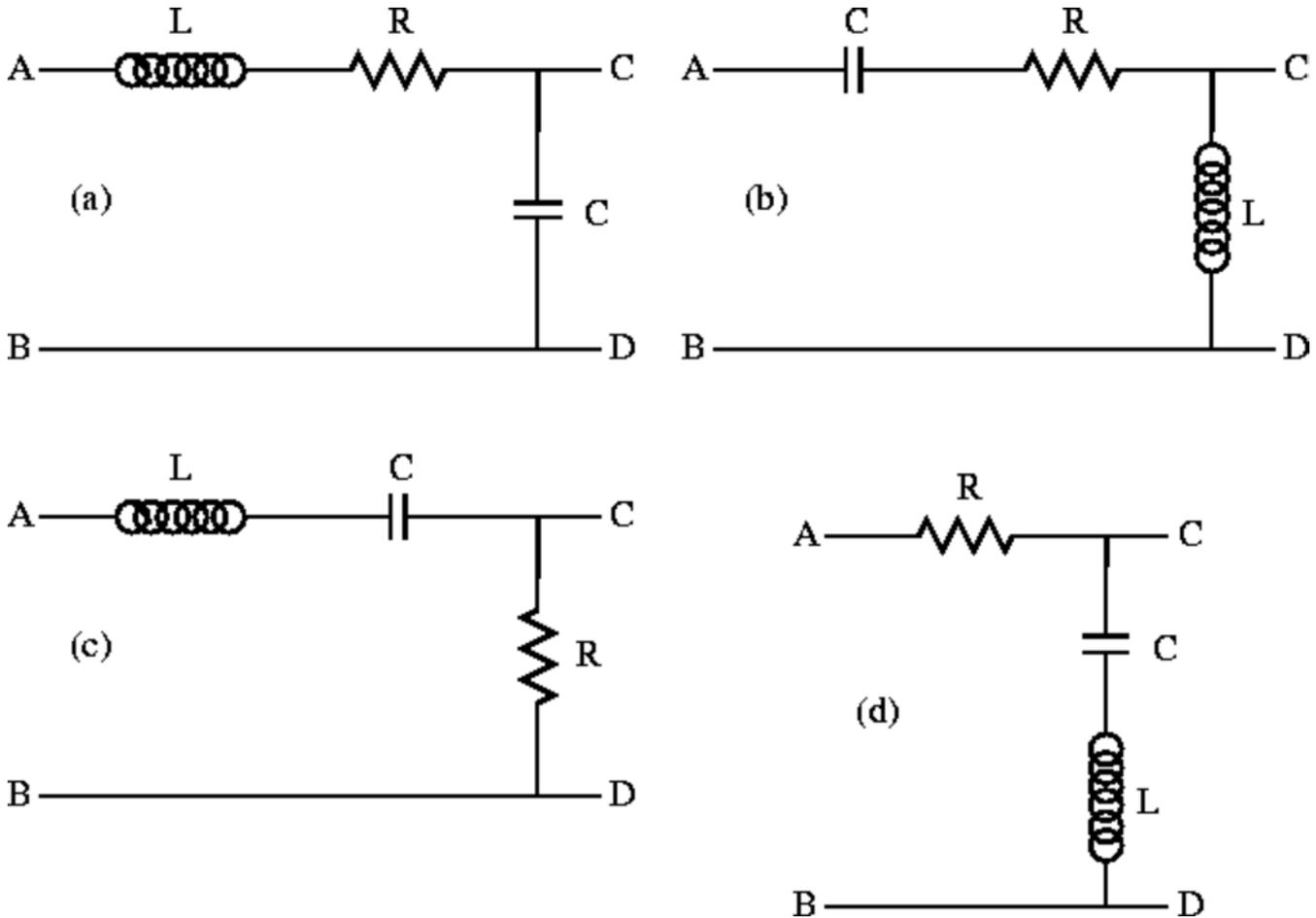


Figure 3.9: LCR filters: a) low-pass, b) high-pass, c) band-pass and d) band-reject.

$$\mathbf{H} = \frac{1/(j\omega C) + j\omega L}{R + 1/(j\omega C) + j\omega L} \quad (3.51)$$

$$= \frac{1 - \omega^2 LC}{(1 - \omega^2 LC) + j\omega RC} \quad (3.52)$$

The approximations are:

$$\omega \rightarrow 0; \quad \mathbf{H} \rightarrow \mathbf{H}_L = 1 \quad \text{and} \quad (3.53)$$

$$\omega \rightarrow \infty; \quad \mathbf{H} \rightarrow \mathbf{H}_H = 1. \quad (3.54)$$

We notice a zero in the transfer function at $\omega_0 = 1/\sqrt{LC}$. In the low-medium frequency range

$$\omega < \omega_0; \quad \mathbf{H} \rightarrow \mathbf{H}_{LM} = \frac{1}{j\omega RC} \propto \omega^{-1}, \quad (3.55)$$

for high-medium frequencies

$$\omega > \omega_0; \quad \mathbf{H} \rightarrow \mathbf{H}_{HM} = \frac{-\omega^2 LC}{j\omega RC} = \frac{j\omega L}{R} \propto \omega^1. \quad (3.56)$$

Solving for the corner frequencies we have

$$1 = 1/|j\omega RC| \Rightarrow \omega_1 = 1/(RC), \quad (3.57)$$

$$1 = |j\omega L/R| \Rightarrow \omega_2 = R/L \text{ and} \quad (3.58)$$

$$\omega_0 = 1/\sqrt{LC} = \sqrt{\omega_1\omega_2}. \quad (3.59)$$

Example: Sketch $|\mathbf{H}(j\omega)|$ for the LCR circuit shown in figure 3.10 for the two conditions $R = 0.5\sqrt{L/C}$ and $R = 2\sqrt{L/C}$. In each case, determine the values of $|\mathbf{H}|$ at $\omega = 0$, ∞ , and ω_0 , and label these points on the sketches.

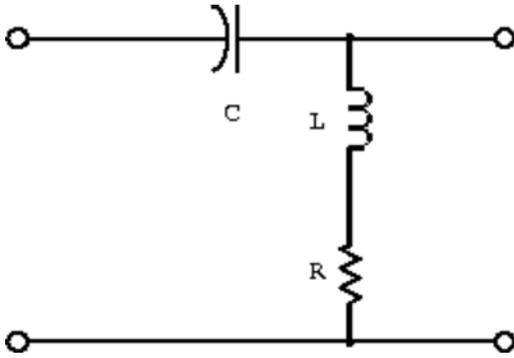


Figure 3.10: LCR circuit with two components across the output.

The transfer function is

$$\mathbf{H}(j\omega) = \frac{R + j\omega L}{R + j\omega L + \frac{1}{j\omega C}}. \quad (3.60)$$

For ω small

$$\mathbf{H}(j\omega) \approx \frac{R}{1/(j\omega C)} = j\omega RC \quad (3.61)$$

$$|\mathbf{H}(j\omega)| = \omega RC. \quad (3.62)$$

For large ω : $\mathbf{H}(j\omega) = 1$.

For the corner frequency: $1 = \omega_0 RC \rightarrow \omega_0 = 1/(RC)$.

For $R = 0.5\sqrt{L/C} = \frac{1}{2}\sqrt{\frac{L}{C}}$,

$$H_{low} = \frac{1}{2}\sqrt{LC}; \omega_0 = \frac{2}{\sqrt{LC}}.$$

$$\mathbf{H}(j\omega_0) = \frac{R + 2j\sqrt{L/C}}{R + 2j\sqrt{L/C} - j/2\sqrt{L/C}} = \frac{R + 4jR}{R + 4jR - jR} \quad (3.63)$$

$$= \frac{1 + 4j}{1 + 3j} = \frac{(1 + 4j)(1 - 3j)}{1 + 9} = \frac{13 + j}{10} \quad (3.64)$$

$$|\mathbf{H}(j\omega_0)| = \sqrt{\frac{13^2 + 1^2}{10^2}} = \sqrt{\frac{170}{10}} = 1.30. \quad (3.65)$$

For $R = 2\sqrt{L/C}$,

$$H_{low} = 2\omega\sqrt{LC}; \omega_0 = \frac{1}{2\sqrt{LC}}$$

$$\mathbf{H}(j\omega C) = \frac{R + j/2\sqrt{L/C}}{R + j/2\sqrt{L/C} - 2j\sqrt{L/C}} = \frac{2 + j/2}{2 + j/2 - 2j} \quad (3.66)$$

$$= \frac{4 + j}{4 - 3j} = \frac{(4 + j)(4 + 3j)}{16 + 9} = \frac{13 + 16j}{25} \quad (3.67)$$

$$|\mathbf{H}(j\omega C)| = \sqrt{\frac{13^2 + 16^2}{25^2}} = \frac{\sqrt{425}}{25} = 0.825. \quad (3.68)$$

Figure 3.11 is a sketch of the transfer functions.

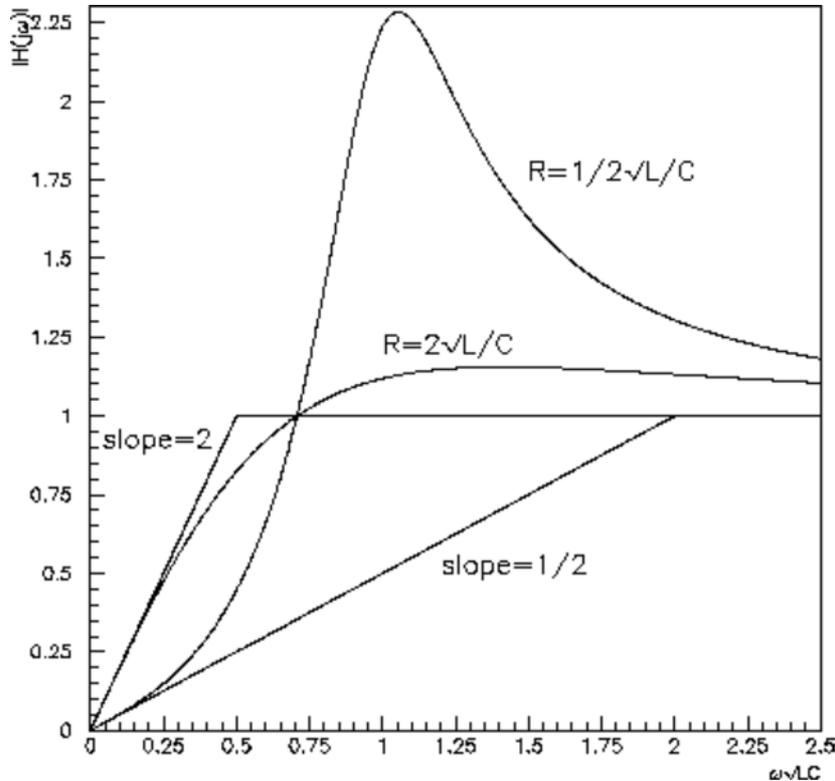


Figure 3.11: Sketch of the transfer functions for the above circuit.

Example:

1. Write an expression for the transfer function of the circuit shown in figure 3.12.

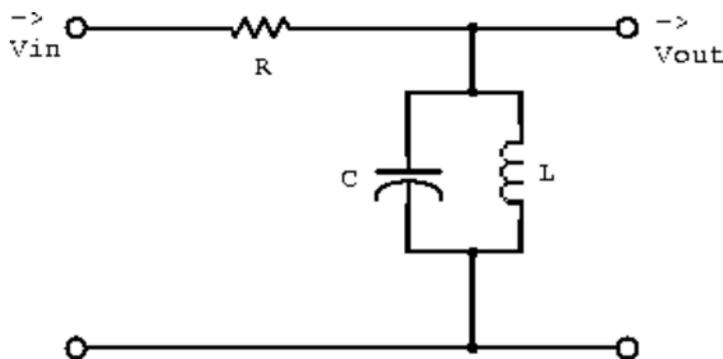


Figure 3.12: Circuit with components in parallel at the output.

$$Z_{CL} = \frac{(1/(j\omega C))(j\omega L)}{1/(j\omega C) + j\omega L} = \frac{j\omega L}{1 - \omega^2 CL} \quad (3.69)$$

$$\mathbf{H}(j\omega) = \frac{\frac{j\omega L}{1 - \omega^2 CL}}{R + \frac{j\omega L}{1 - \omega^2 CL}} = \frac{1}{1 - jR/(\omega L)(1 - \omega^2 CL)} \quad (3.70)$$

$$= \frac{1}{1 + j\left(\omega RC - \frac{1}{\omega L}\right)}. \quad (3.71)$$

2. What phase shift is introduced by this filter at very small and very large frequencies?

For large ω $\mathbf{H}(j\omega) \approx \frac{1}{j\omega RC} = \frac{1}{RC} \omega^{-1}$

$$\mathbf{H}_{high} = \frac{1}{RC} \omega^{-1} e^{-j\pi/2} \rightarrow \phi_H = -\frac{\pi}{2}. \quad (3.72)$$

For small ω $\mathbf{H}(j\omega) \approx \frac{1}{(j\omega)(R/L)} = j\omega \frac{L}{R}$

$$\mathbf{H}_{low} = \frac{L}{R} \omega e^{j\pi/2} \rightarrow \phi_L = +\frac{\pi}{2}. \quad (3.73)$$

3. On a log-log scale, sketch $|\mathbf{H}(j\omega)|$ and the phase shift as a function of ω .

For the corner frequency $\omega_C^2 RC = \frac{R}{L} \rightarrow \omega_C = \frac{1}{\sqrt{LC}}$.

$\mathbf{H}(j\omega_C) = 1; \phi_C = 0$.

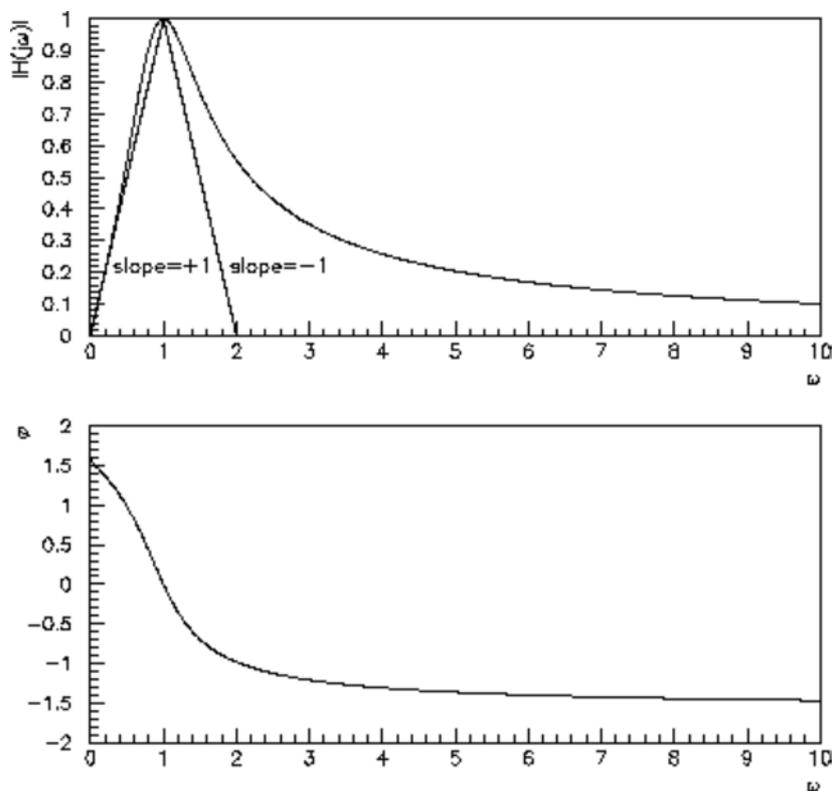


Figure 3.13: Transfer function and phase shift for the above circuit.

[Doug Gingrich](#)

Tue Jul 13 16:55:15 EDT 1999